





# COMPONENTS OF ROBOTS (1)




Resistors

Switch

Breadboard

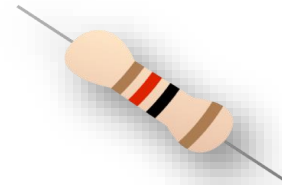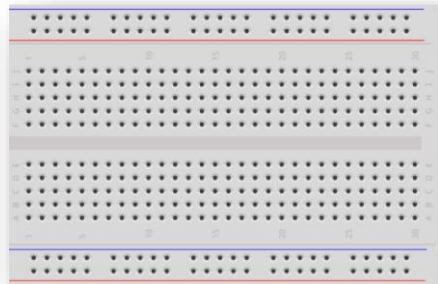


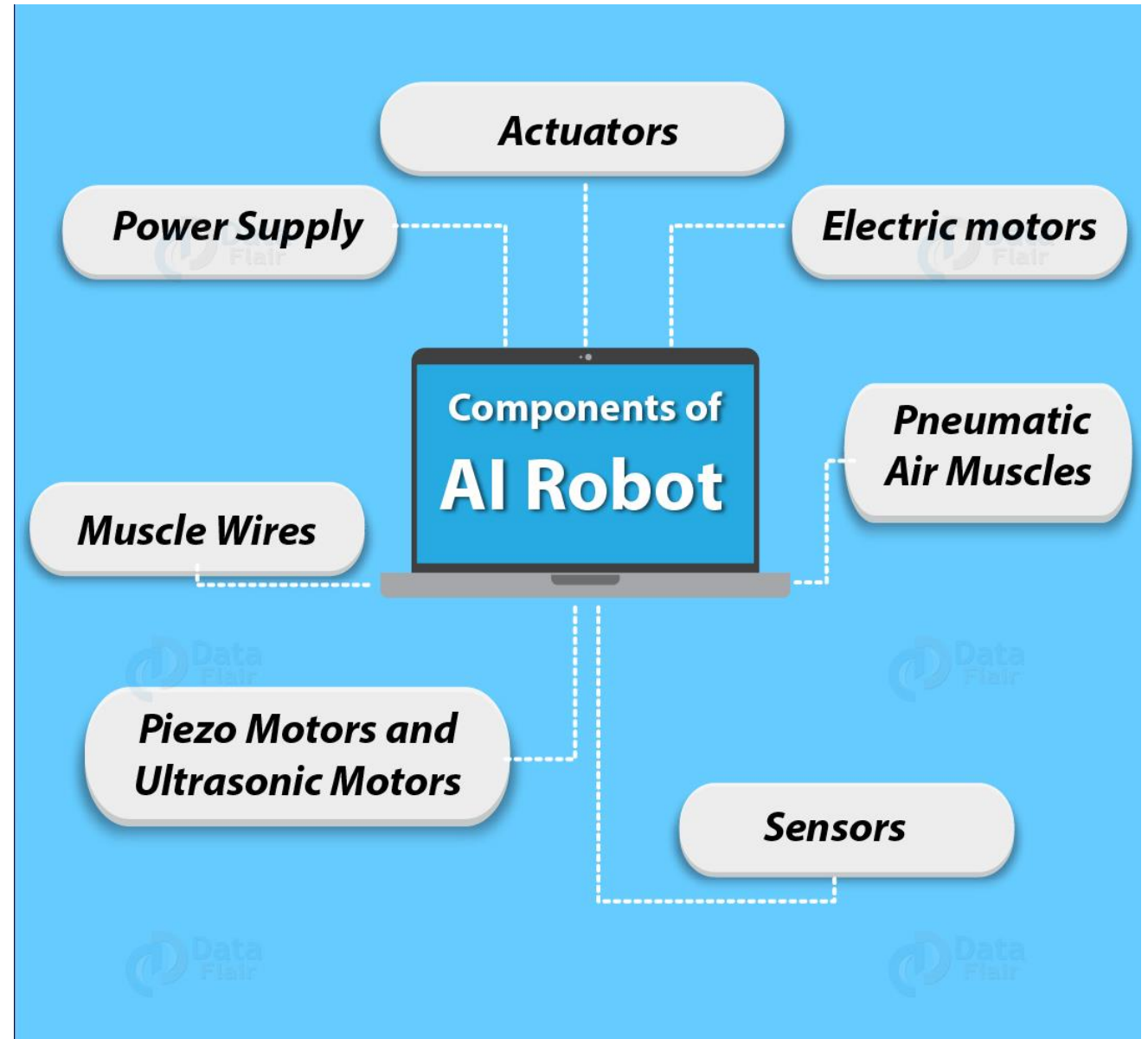
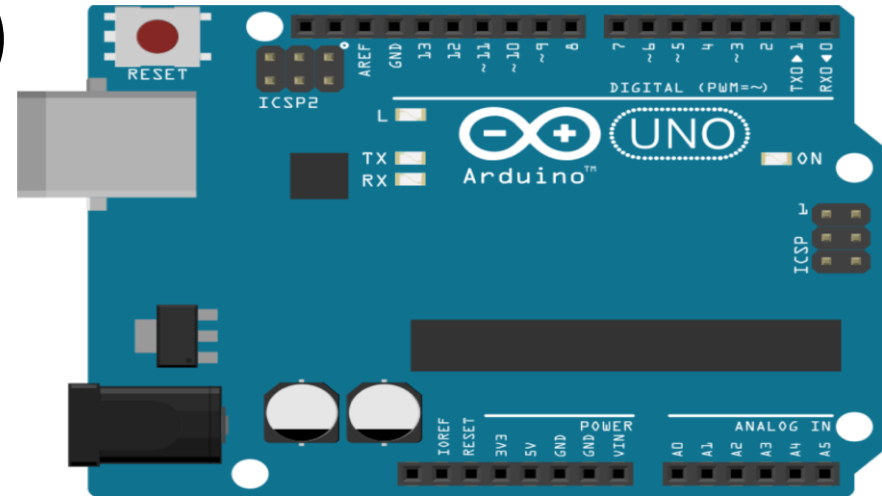
# What do you need?

To get started you need the following:

- PC (Windows, Mac, Linux)
- **Arduino UNO** (~200 NOK)  
or a Starter Kit (~800 NOK)
- Software (free)
- Electrical components  
(wires, resistors, etc.)



## Components of a Robot

Robots are constructed with the following –

**Power Supply** – The robots are powered by batteries, solar power, hydraulic, or pneumatic power sources.

**Actuators** – They convert energy into movement.

**Electric motors (AC/DC)** – They are required for rotational movement.


**Pneumatic Air Muscles** – They contract almost 40% when air is sucked in them.

**Muscle Wires** – They contract by 5% when electric current is passed through them.

**Piezo Motors and Ultrasonic Motors** – Best for industrial robots.


**Sensors** – They provide knowledge of real time information on the task environment. Robots are equipped with vision sensors to be to compute the depth in the environment. A tactile sensor imitates the mechanical properties of touch receptors of human fingertips.

# Equipment

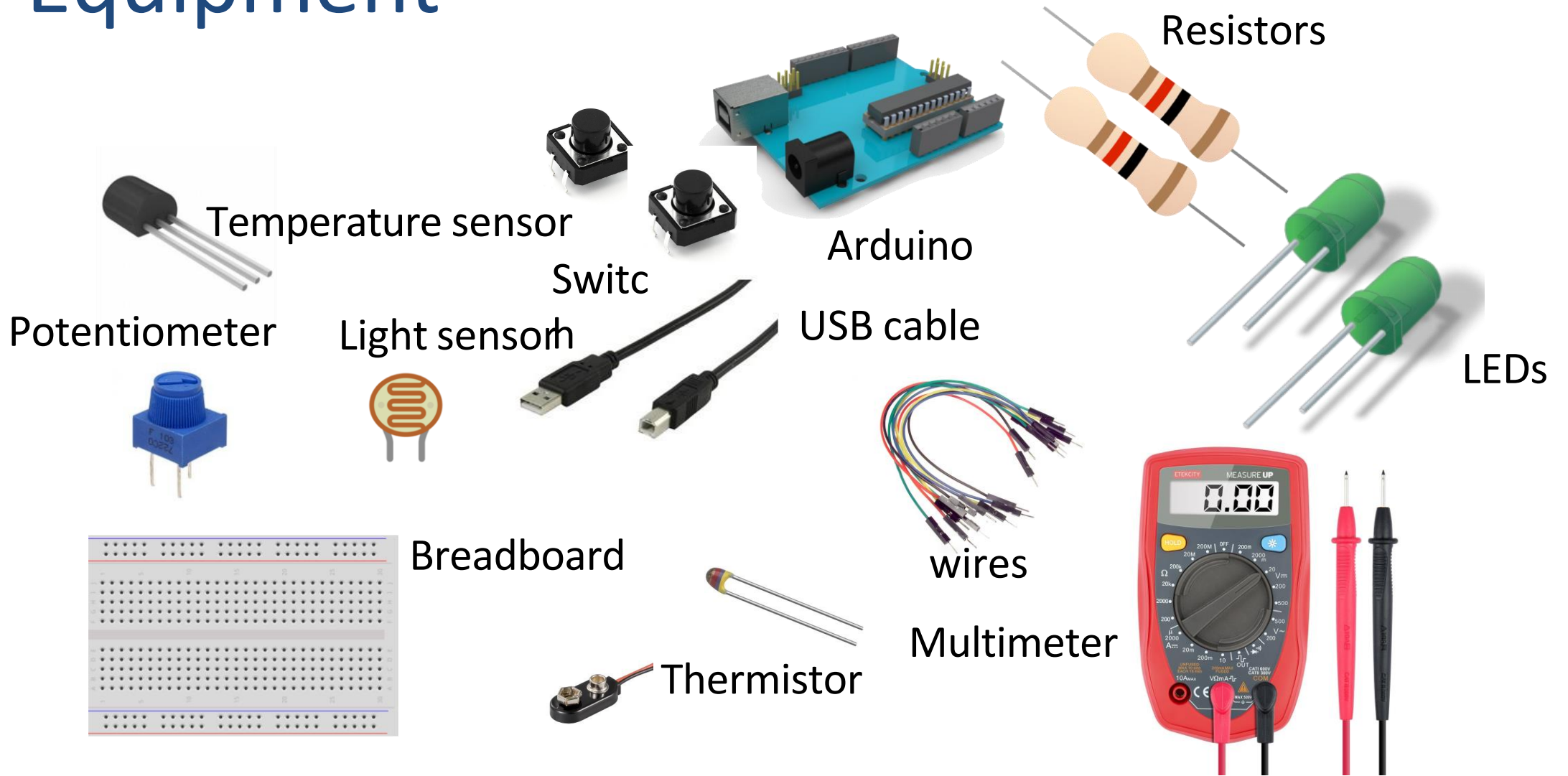



(wires, resistors, etc.)

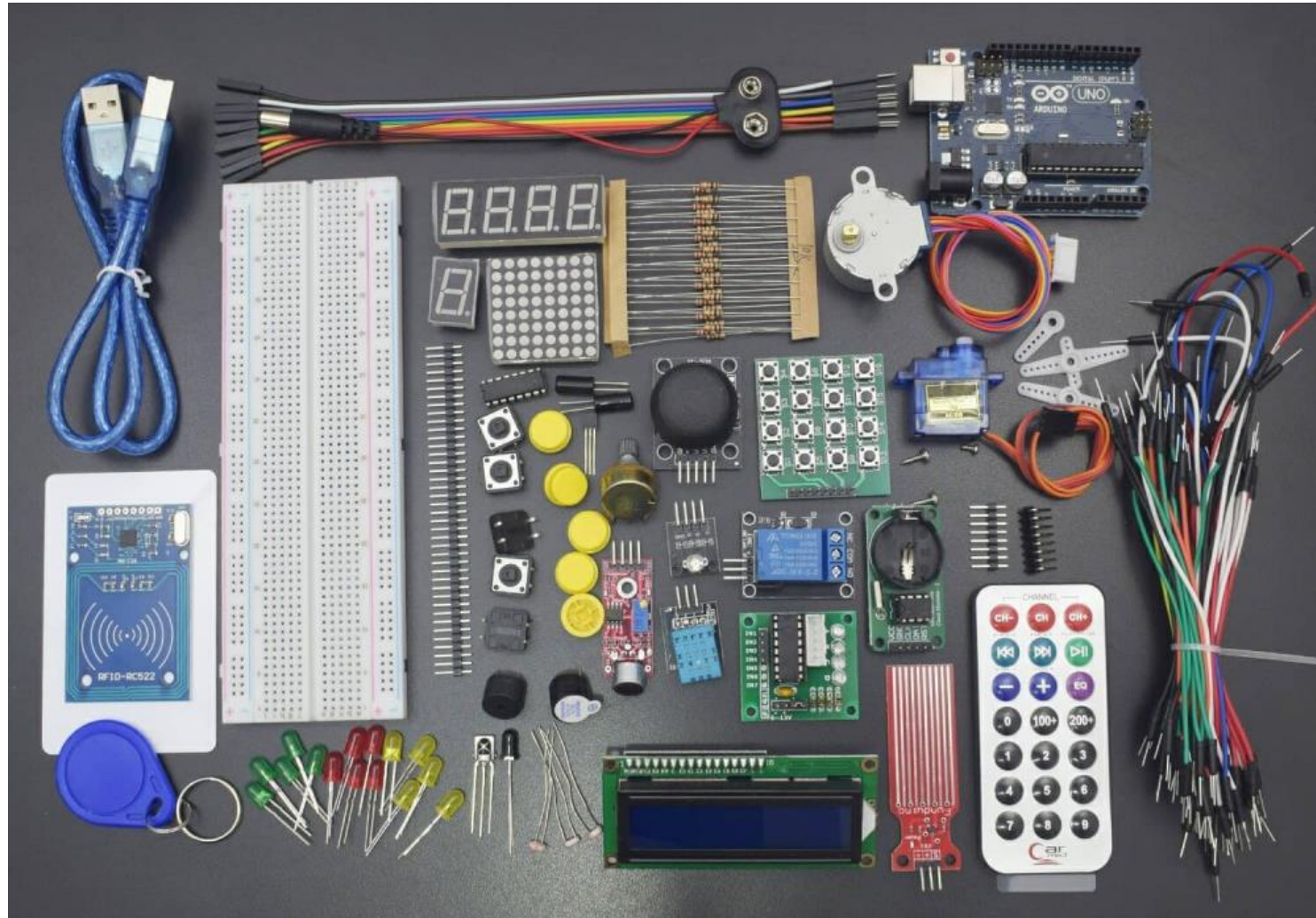


# Resistors

Resistance is measured in Ohm ( $\Omega$ )

Resistors comes in many sizes, e.g.,  $220\Omega$  ,  $270\Omega$ ,  $330\Omega$ ,  $1k\Omega$  to  $10k\Omega$ , ...

The resistance can be found using Ohms Law

$$V = RI$$

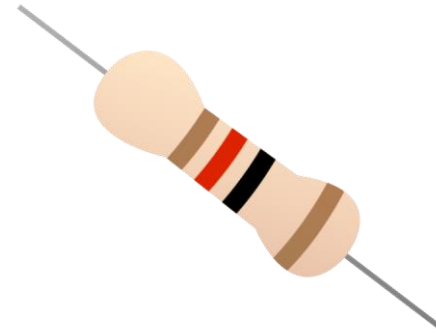

<https://en.wikipedia.org/wiki/Resistor>


Electrical symbol: 

# Ohms Law

This is Ohms Law:

$$V = RI$$

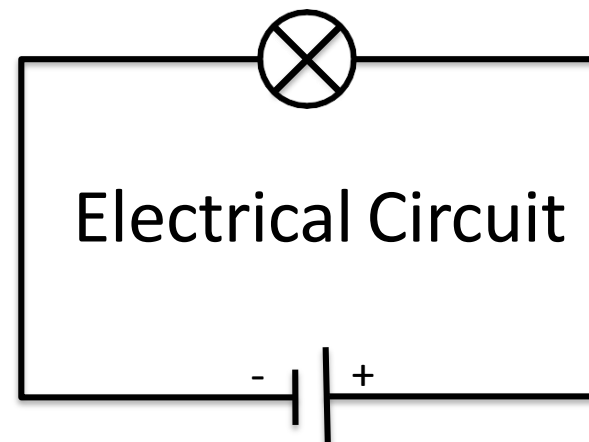$V$  – Voltage [V] **volt**  
 $R$  – Resistance [ $\Omega$ ] **ohm**  
 $I$  – Current [A] **ampere**



• **I**: التيار الكهربائي Electrical Current (أمبير) Ampere  
• **V**: الجهد الكهربائي Electrical Voltage (فولت) Volt  
• **R**: المقاومة الكهربائية Electrical Resistance (أوم)  $\Omega$  Ohm




# Ohms Law

$$V = RI$$

$$R = \frac{V}{I}$$

$$I = \frac{V}{R}$$

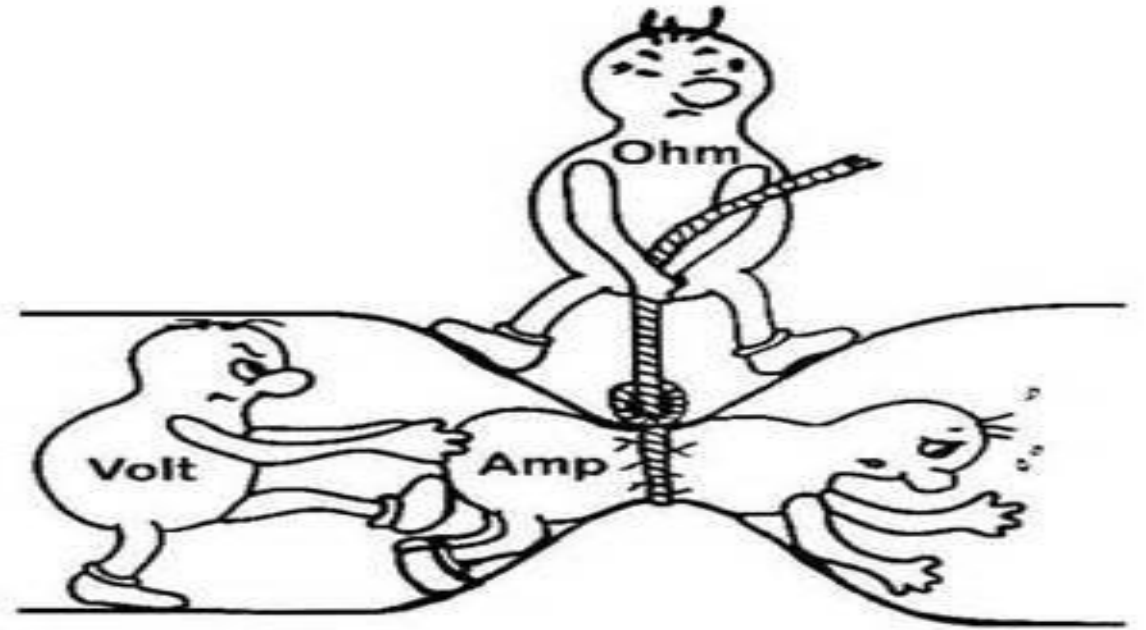


لفهم هذه المعادلة ، سنأخذ المثال التالي ، بطارية 1.2 فولت تم توصيلها إلى مقاومة 220 أوم

التيار الكهربائي يساوي الجهد قسمة المقاومة

$$I = \frac{V}{R}$$
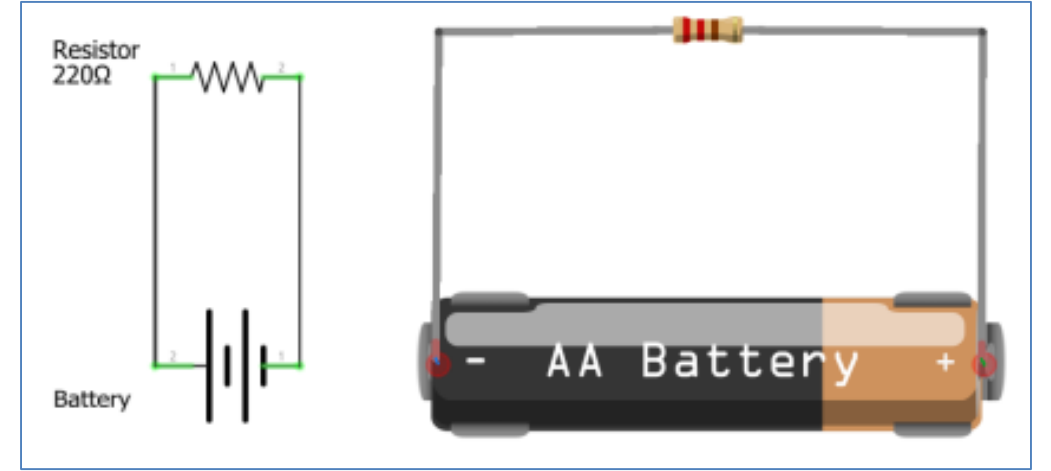
$$I = \frac{1.3}{220} \approx 0.0059 \text{ Ampere} \approx 5.9 \text{ mA}$$




لمعرفة التيار الكهربائي الذي يمر من خلال هذه المقاومة.

• الجهد Voltage يساوي 1.2 فولت Volts

• المقاومة تساوي 220 أوم  $\Omega$

## How to find out the resistance value

$$R = \frac{V}{I}$$

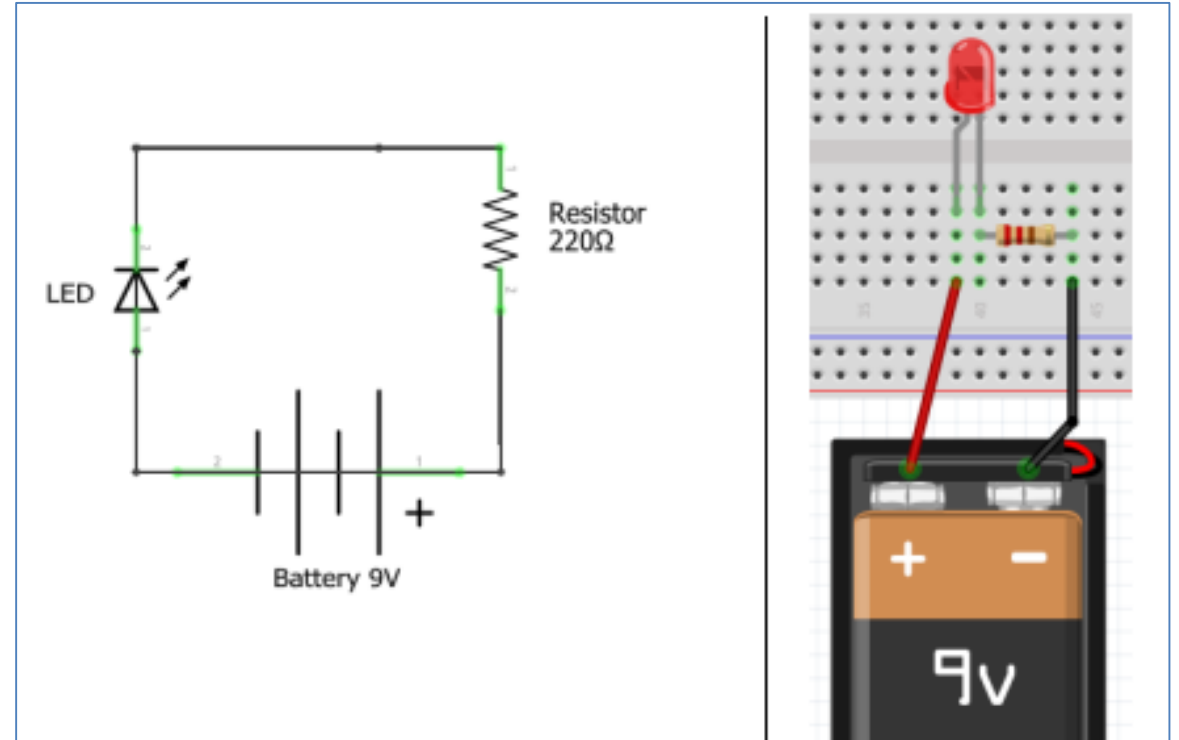

قيمة المقاومة = ( فولتاج البطارية - فولتاج الثنائي الضوئي ) / ( تيار الثنائي الضوئي )

$$350 \text{ أوم } \Omega = (0.02) / (2 - 9) =$$

# Resistor Color Codes

- What is the values for your resistors?
- Use the Color Codes to figure it out
- Use also a Multimeter to see if you get the same results.



# Multimeter

You can use a Multimeter to measure current, voltage, resistance, etc. in an electric circuit.



<https://learn.sparkfun.com/tutorials/how-to-use-a-multimeter>

# Resistor Color Codes

2%, 5%, 10%

4-Band-Code


560k  $\Omega$   $\pm$  5%

COLOR	1 <sup>ST</sup> BAND	2 <sup>ND</sup> BAND	3 <sup>RD</sup> BAND	MULTIPLIER	TOLERANCE
Black	0	0	0	1 $\Omega$	
Brown	1	1	1	10 $\Omega$	$\pm$ 1% (F)
Red	2	2	2	100 $\Omega$	$\pm$ 2% (G)
Orange	3	3	3	1K $\Omega$	
Yellow	4	4	4	10K $\Omega$	
Green	5	5	5	100K $\Omega$	$\pm$ 0.5% (D)
Blue	6	6	6	1M $\Omega$	$\pm$ 0.25% (C)
Violet	7	7	7	10M $\Omega$	$\pm$ 0.10% (B)
Grey	8	8	8		$\pm$ 0.05%
White	9	9	9		
Gold				0.1 $\Omega$	$\pm$ 5% (J)
Silver				0.01 $\Omega$	$\pm$ 10% (K)

0.1%, 0.25%, 0.5%, 1%


5-Band-Code

237  $\Omega$   $\pm$  1%

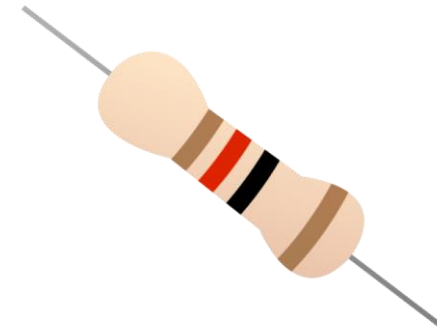
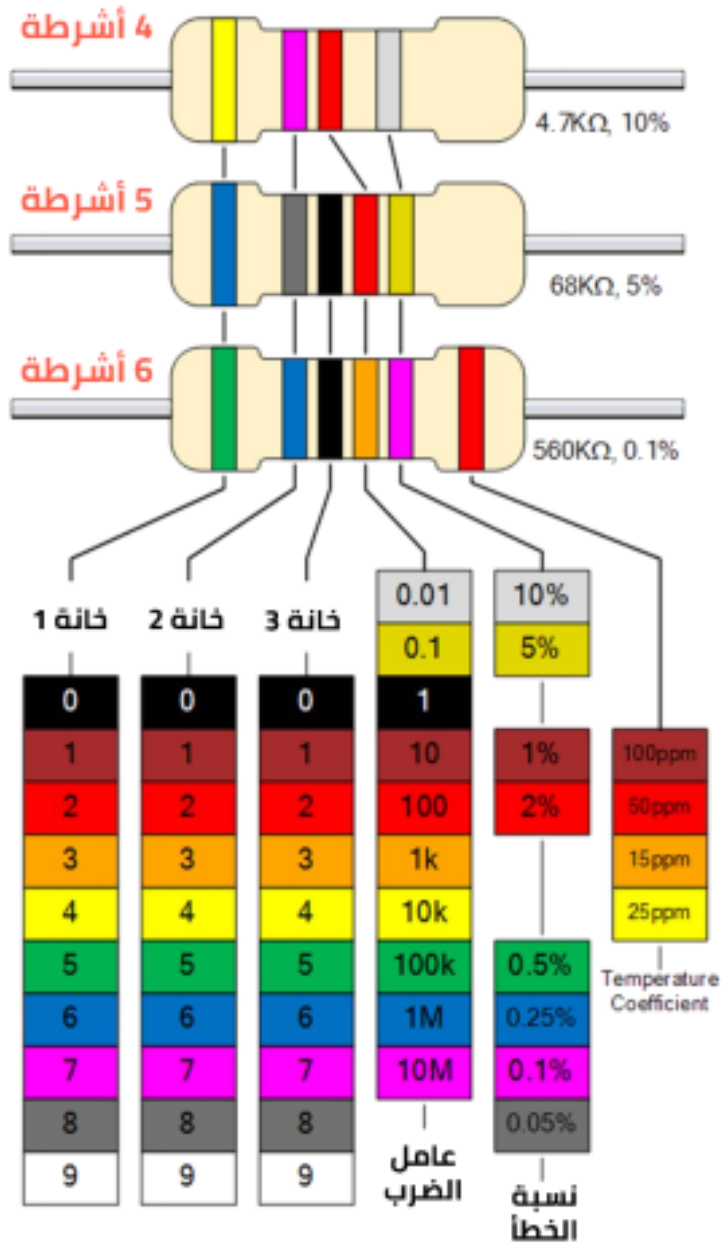
<http://www.allaboutcircuits.com/tools/resistor-color-code-calculator/>






الشريط 1 (خانة 1) : بني				
الشريط 2 (خانة 2): أسود				
الشريط 3 (عامل الضرب): أحمر				
الشريط 4 (نسبة الخطأ): ذهبي				
نسبة الخطأ	أحمر	X	أسود	بني
5%	100	X	0	1
5%	100	X	10	
5%	1000 $\Omega$			
5%	1 K $\Omega$			


  

الشريط 1 (خانة 1) : أحمر				
الشريط 2 (خانة 2): أحمر				
الشريط 3 (عامل الضرب): بني				
الشريط 4 (نسبة الخطأ): ذهبي				
نسبة الخطأ	بني	X	أحمر	أحمر
5%	10	X	2	2
5%	10	X	22	
5%	220 $\Omega$			

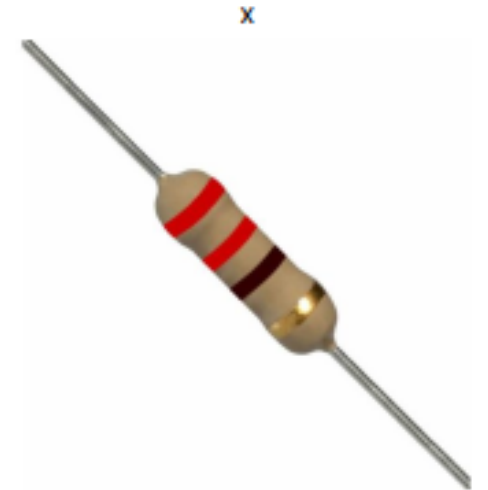

# Resistors in Series and Parallel


## Resistors in Series:

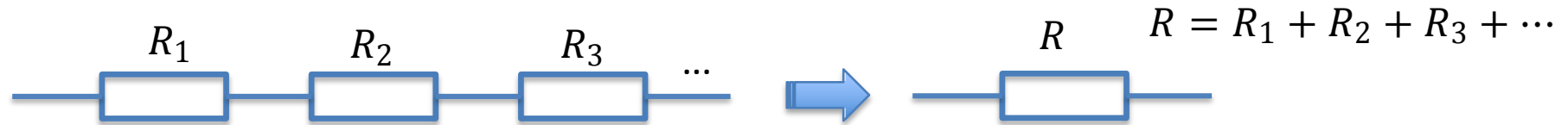

The total resistance of resistors connected in series is the sum of their individual resistance values.

When we have resistors in series, the sum of the sub-voltages is equal to the voltage of the voltage source

## Resistors in Parallel :

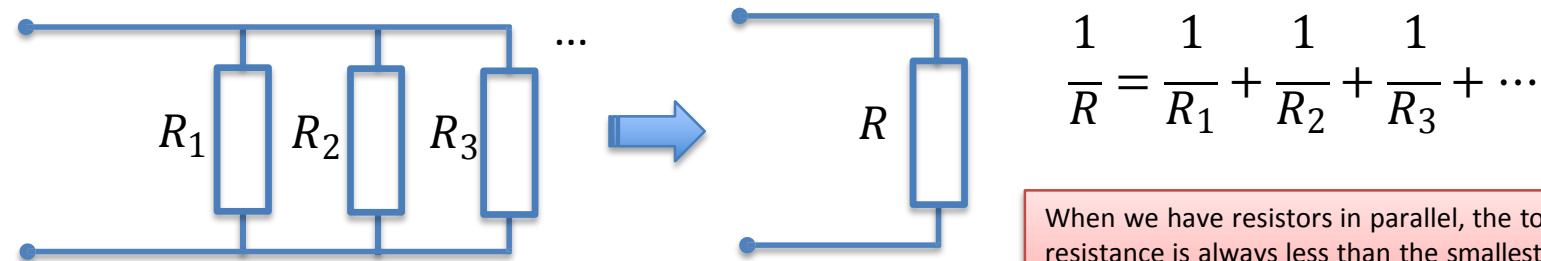


When we have resistors in parallel, the total resistance is always less than the smallest resistors

# Kirchhoff's Laws

## Kirchhoff's Current Law:

$$\sum_{K=1}^n I_k = 0$$

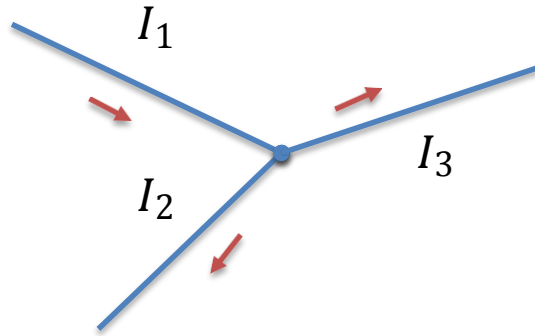


$$I_1 = I_2 + I_3$$

$$I_1 - I_2 - I_3 = 0$$

## Kirchhoff's Voltage Law:

$$\sum_{K=1}^n U_k = 0$$

$$U = U_1 + U_2 + U_3 + \dots$$

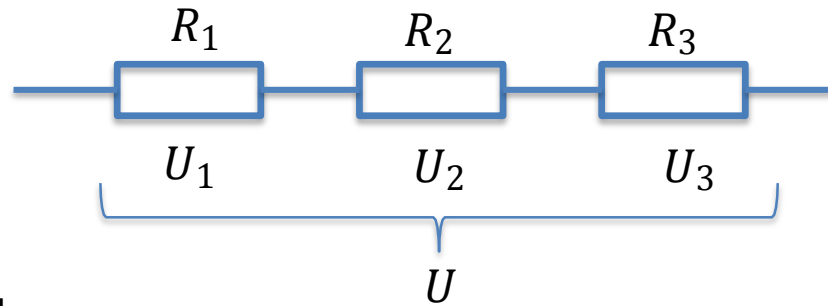


[https://en.wikipedia.org/wiki/Kirchhoff%27s\\_circuit\\_laws](https://en.wikipedia.org/wiki/Kirchhoff%27s_circuit_laws)

# Switch

A switch breaks the flow of current through a circuit when open. When closed, the current will flow unobstructed through the circuit.





A switch comes in many flavors

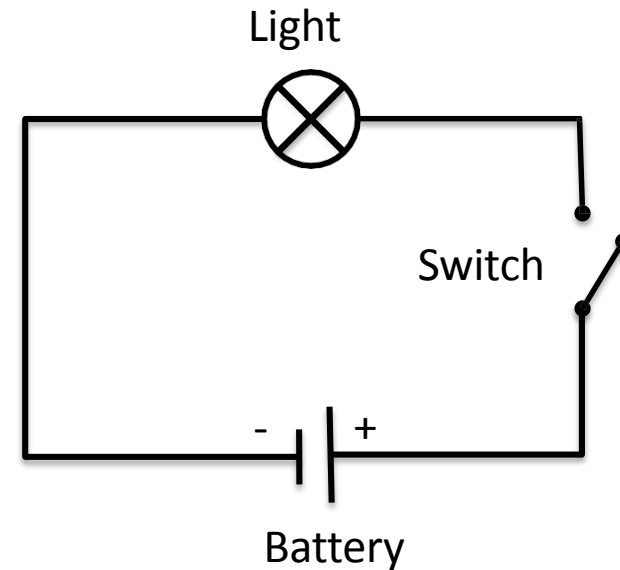


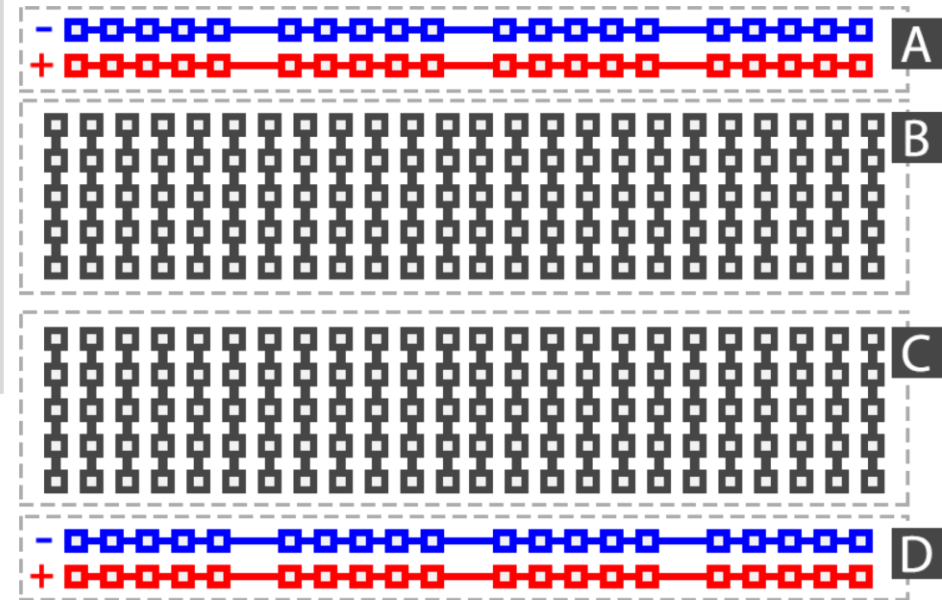
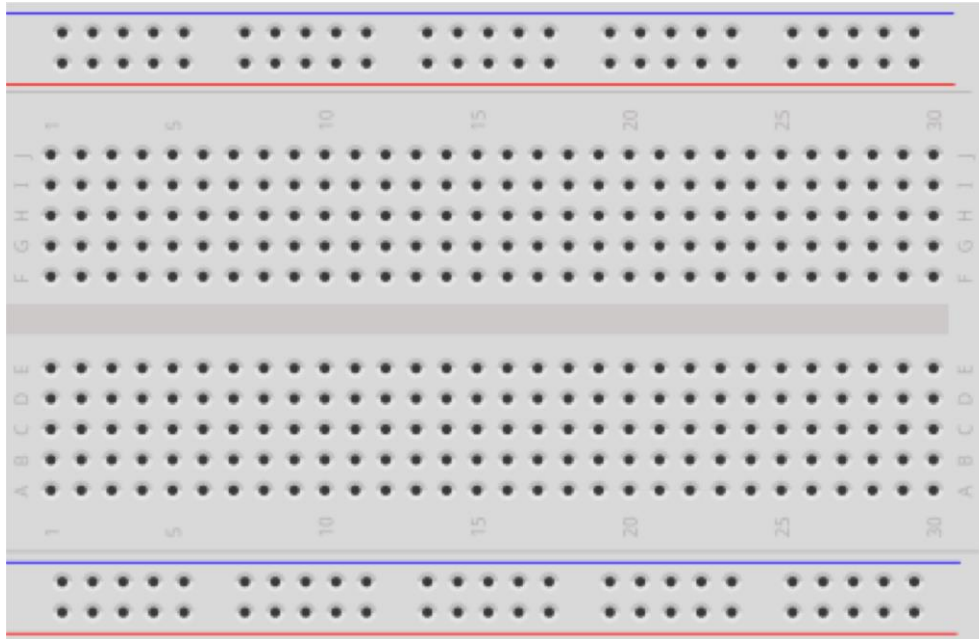
# Breadboard

A breadboard is used to wire electric components together



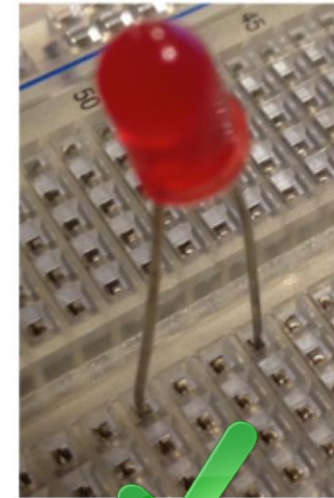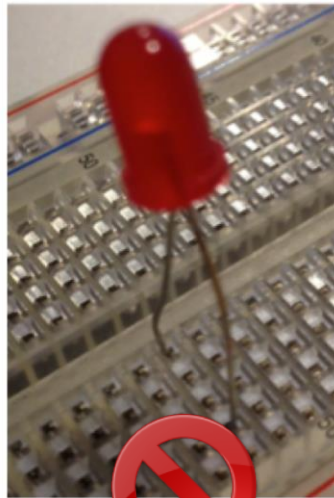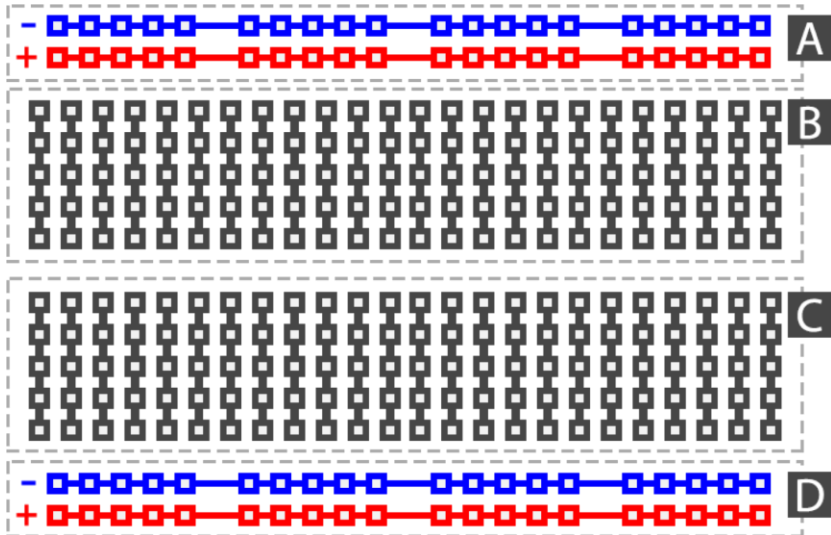
# Breadboard – Correct Wiring

Make sure not to short-circuit the components that you wire on the breadboard







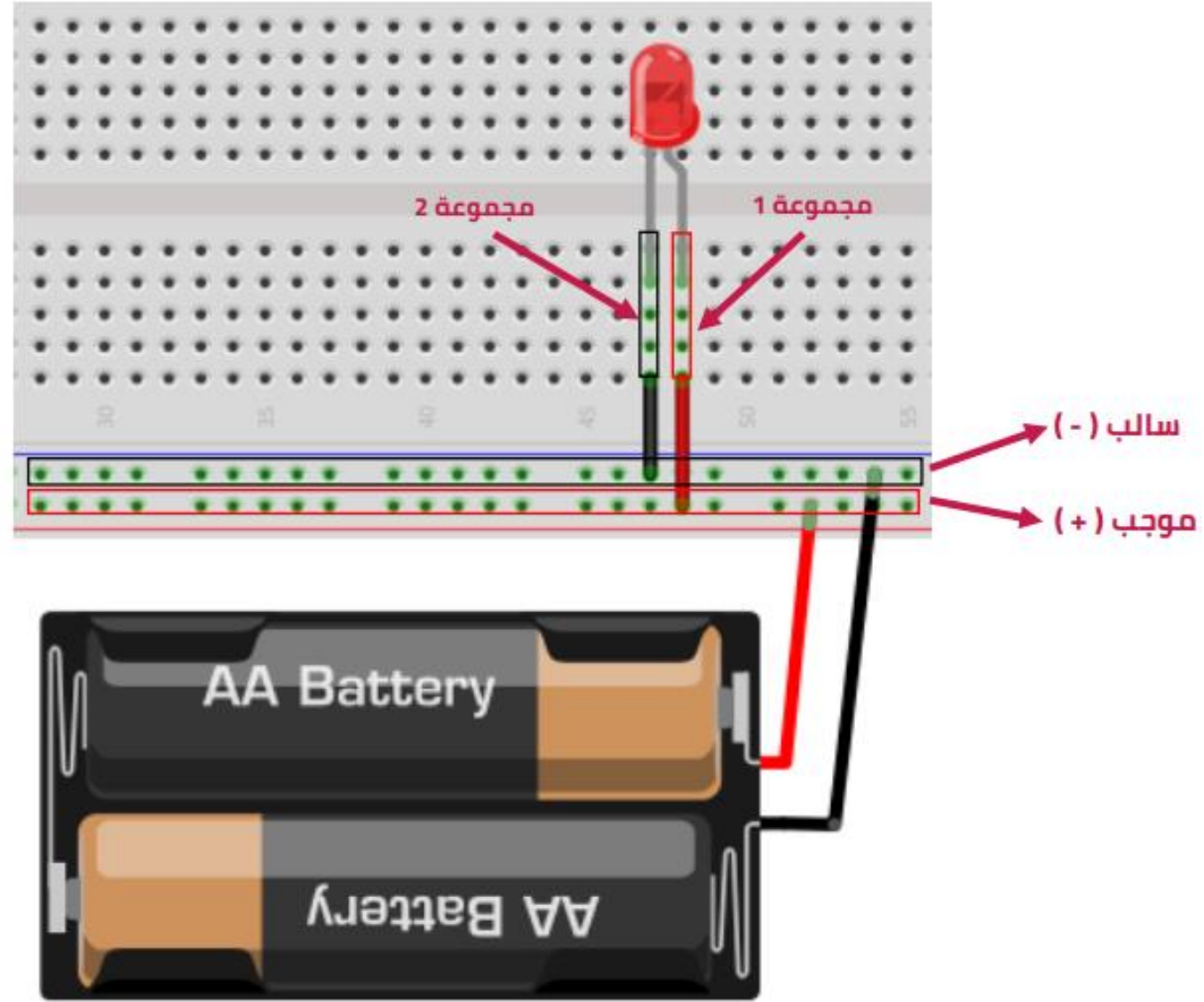

# Electronics Foundation



# Electrical Circuit

Here you see a basic Electrical Circuit:

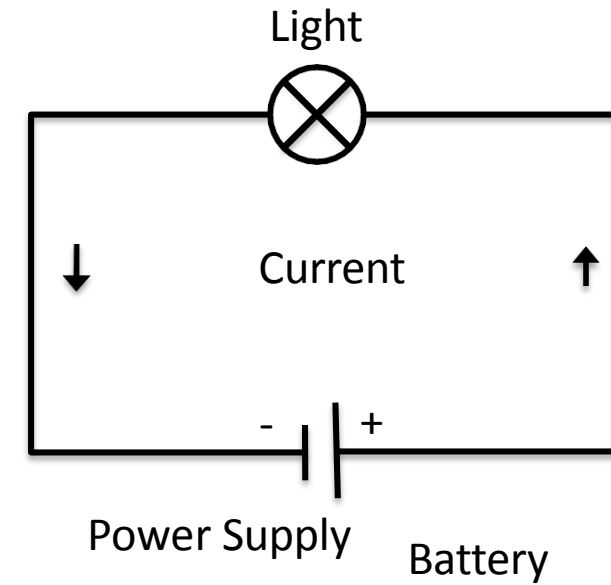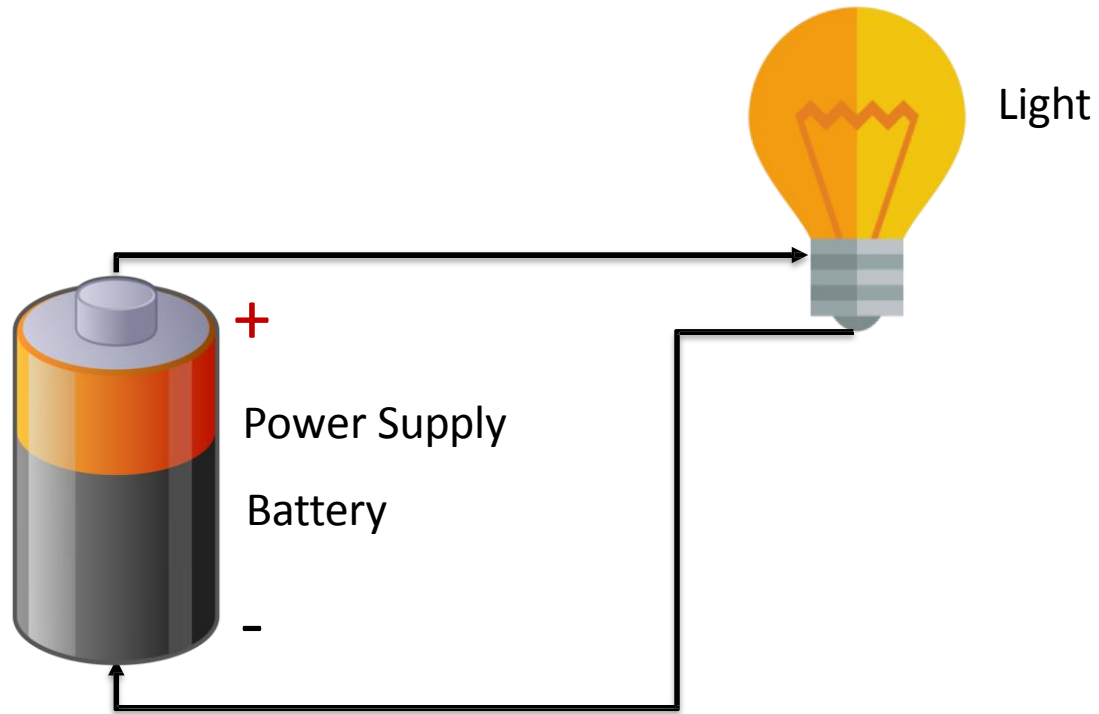

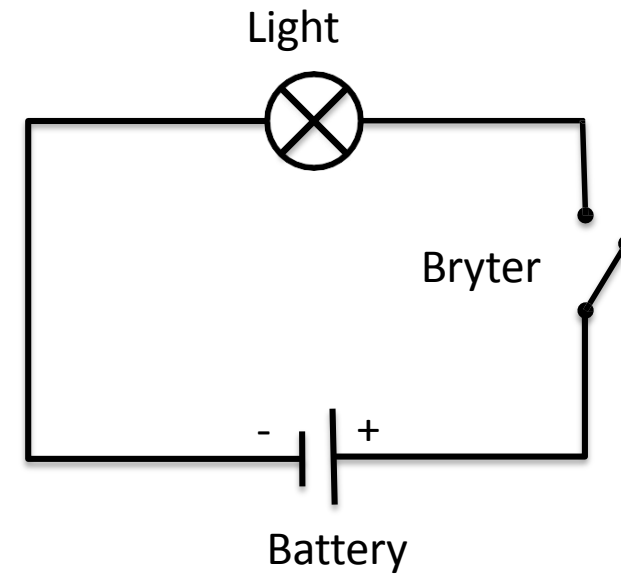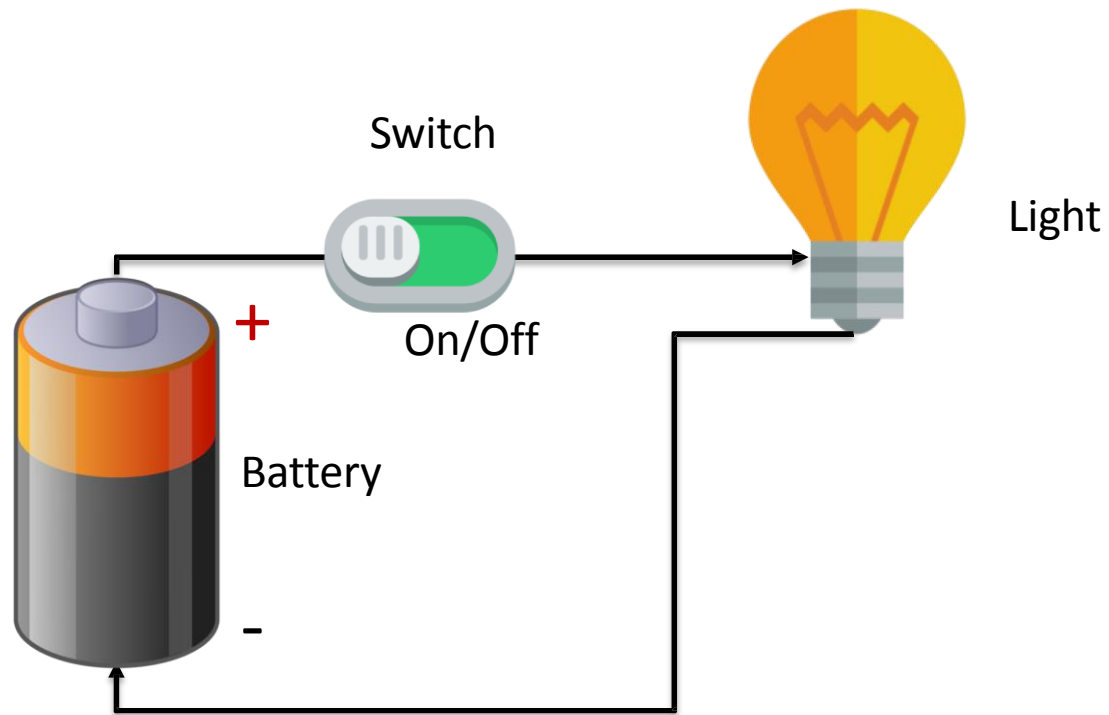
# Electrical Circuit with a Switch

Here you see a basic Electrical Circuit with a Switch:





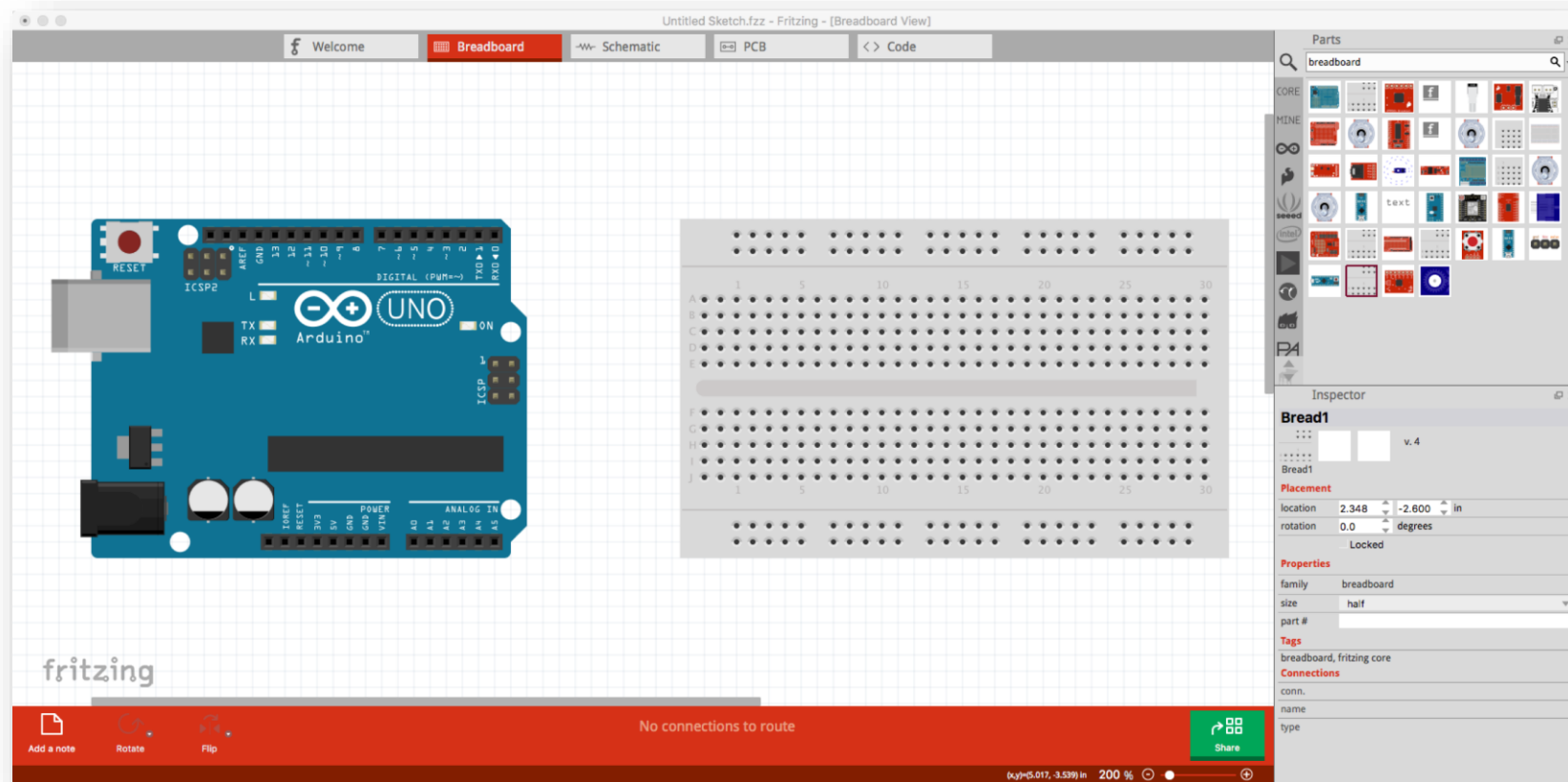Fritzing is an **open-source hardware initiative** that makes electronics accessible as a creative material for anyone.




[\[http://www.fritzing.org\]](http://www.fritzing.org)

# Short Circuit




- We must never connect positive and negative side to a power source without having an electrical component in between.
- If you do, it is called a short circuit.
- For example, if you short circuit a battery, the battery will get very hot and the battery will run out very quickly.
- Some batteries may also start to burn.
- When it starts to smoke from electrical components, it happens because it has become too hot.
- In most cases, it means that the component is broken.

Short Circuit!!

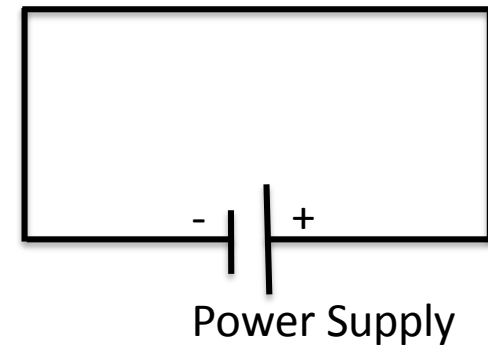



# Light-Emitting Diode - LED

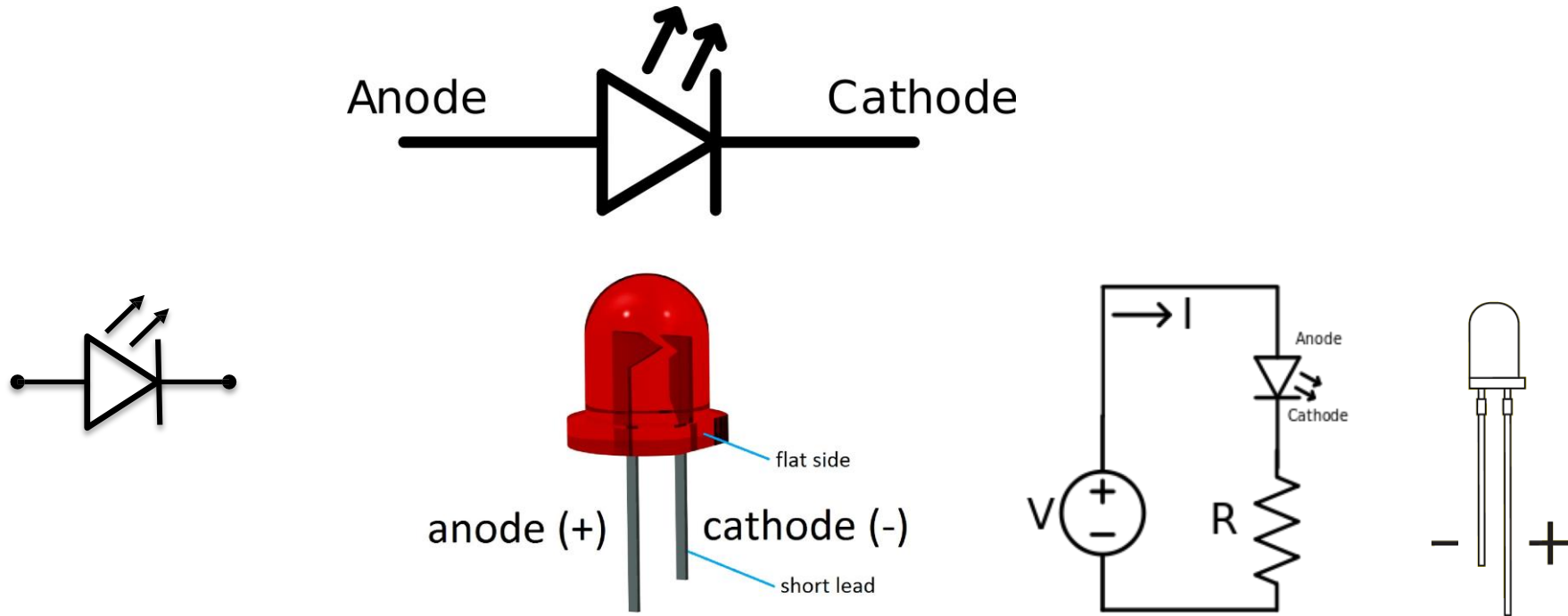

[Wikipedia]